

# Report For VHDL Project

\*HalfAdder: to sum 2bits.

\*FullAdder: to sum 3bits.

\*RCA: to sum n-bit+n-bit

## First Stage:

### -Idea:

We want to add 3 numbers x,y,z in s,c

we declare x,y,z,s,c as bit\_vector with size 4 bits

Then we add each column and the sum append to s and the carry append to c

Like this:

we add the first right bit x,y,z and add it in s and carry in c

Like this  $x(0)+y(0)+z(0)=s(0)$  and  $c(0)$

$x(1)+y(1)+z(1)=s(1)$  and  $c(1)$

$x(2)+y(2)+z(2)=s(2)$  and  $c(2)$

$x(3)+y(3)+z(3)=s(3)$  and  $c(3)$


and because we added 3 bits we will use FullAdder

Conclusion we need 4FullAdders in this stage.


### - InCoding:

1.Implement FullAdder Entity using two instances from HalfAdder Entity.


\*\*HalfAdder:

 


\*\*FullAdder:

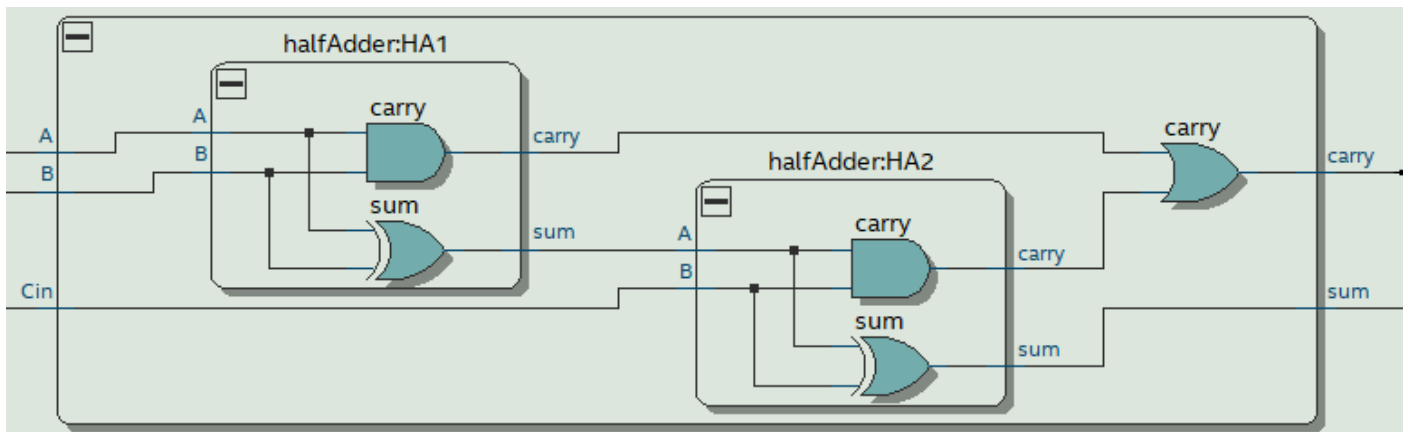

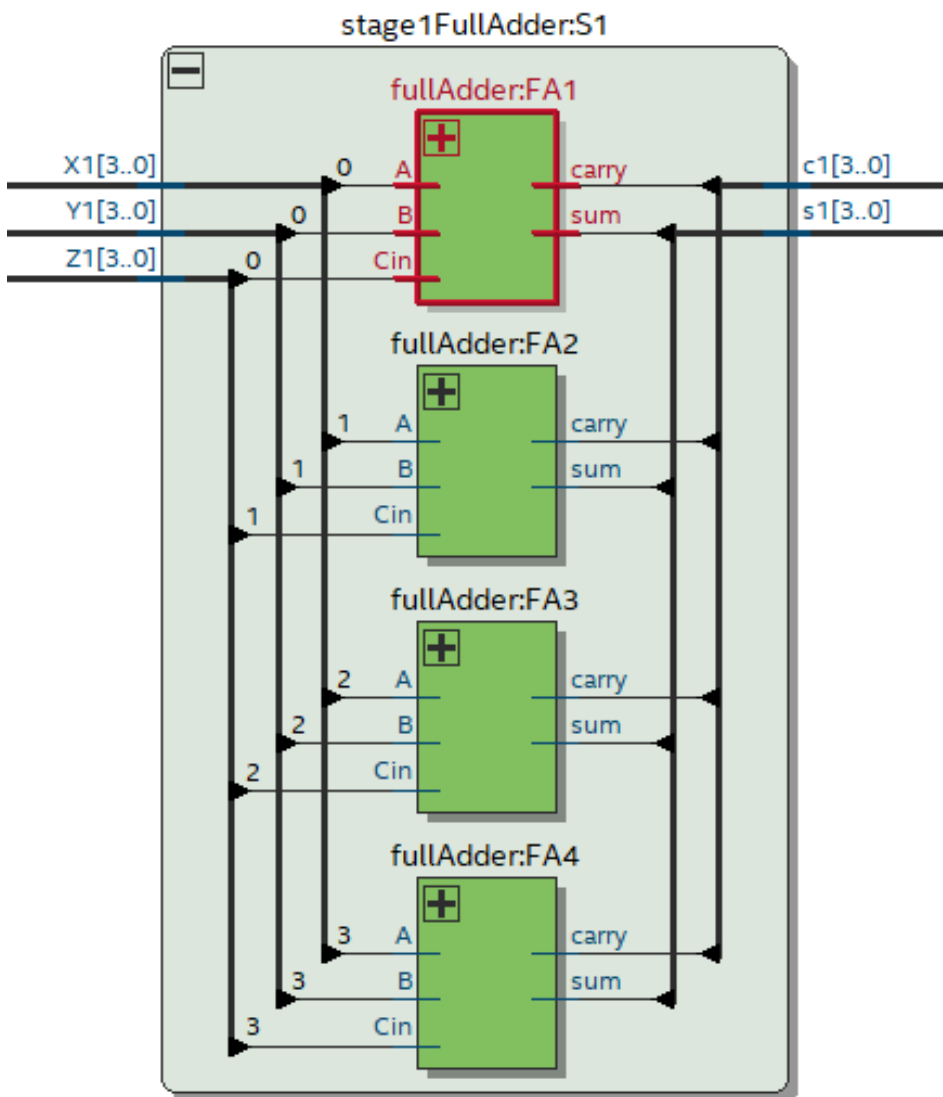2.Implement stage1 by using 4instances from FullAdder:



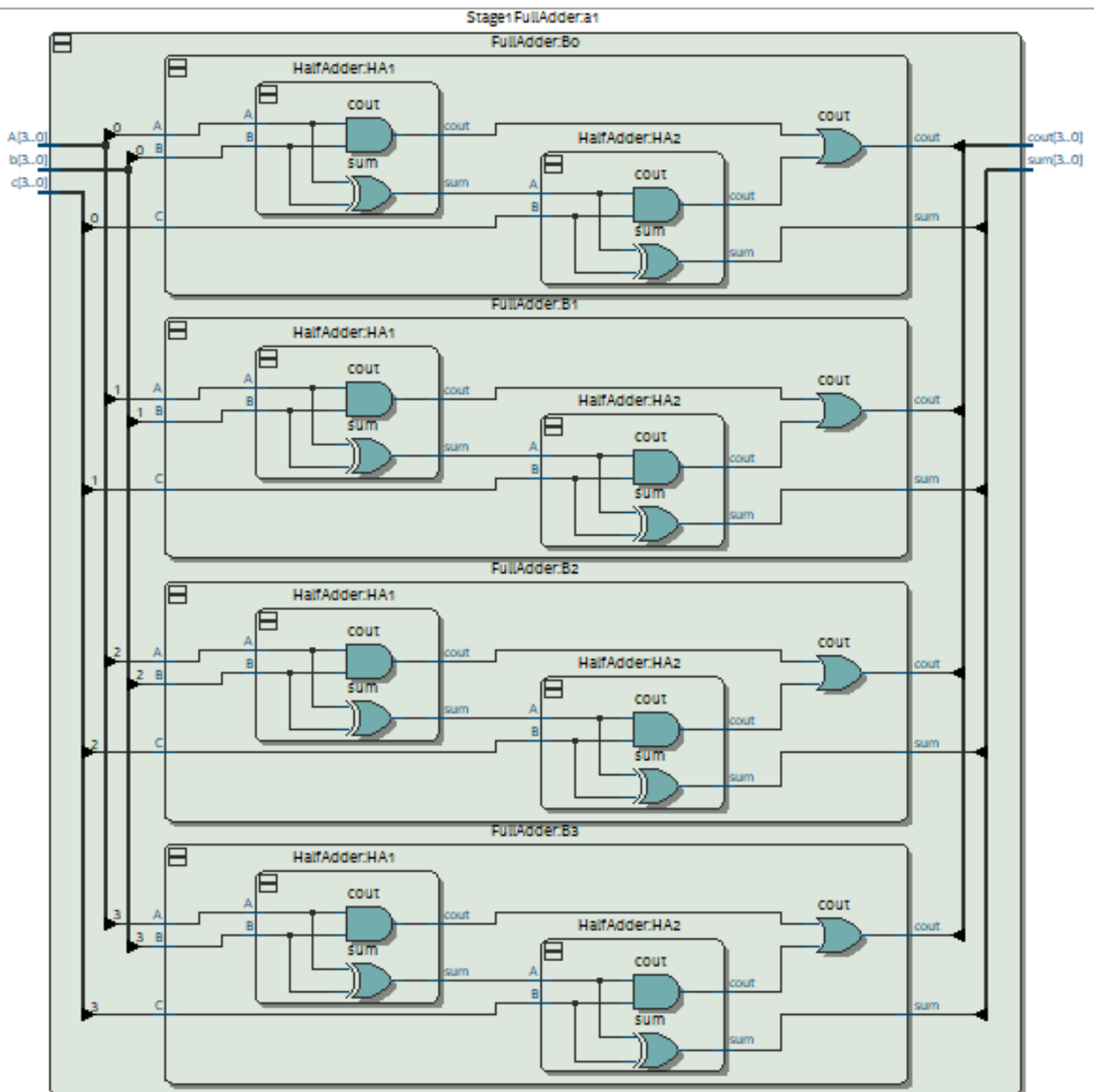

Stage1 is done.

## Second Stage:

We have 2bit\_vector s,c with size 4bit

And declare bit\_vector sum with size 5bit ,one bit carry.

**-idea:**

1. keep the first left bit in s the same because it isn't have carry to add

$$\text{Sum}(0) \leq s(0)$$

2. add the next bit (second bit) in s with the first bit in carry, and put the carry in c1(it is a signal to connect the next step)

$$\text{Sum}(1) \leq s(1) + c(0) + '0' \text{ (no additional carry)}$$

3. add the third bit in s with the second bit in carry and the c1 from previous step, and put the carry in c2(it is a signal to connect the next step)

$$\text{Sum}(2) \leq s(2) + c(1) + c1$$

4. add the fourth bit in s with the third bit in carry and the c2 from previous step, and put the carry in c3(it is a signal to connect the next step)

$$\text{Sum}(3) \leq s(3) + c(2) + c2$$


Step 2 and 3 and 4 can do it by using RCA\_3bit

(RCA\_3bit contains 3FullAdders)

5. Then we will use HalfAdder to sum the c3(from previous step) and the last bit in carry c(3)


The output s from HA is sum(4)


And the carry is the final carry

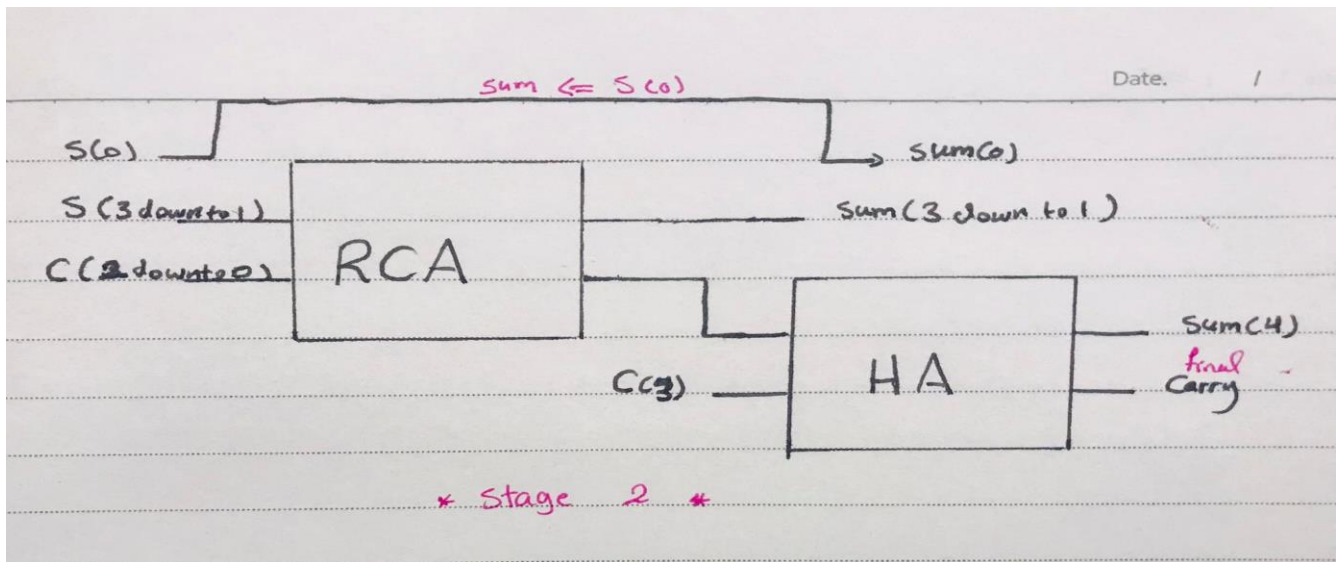

## - InCoding:

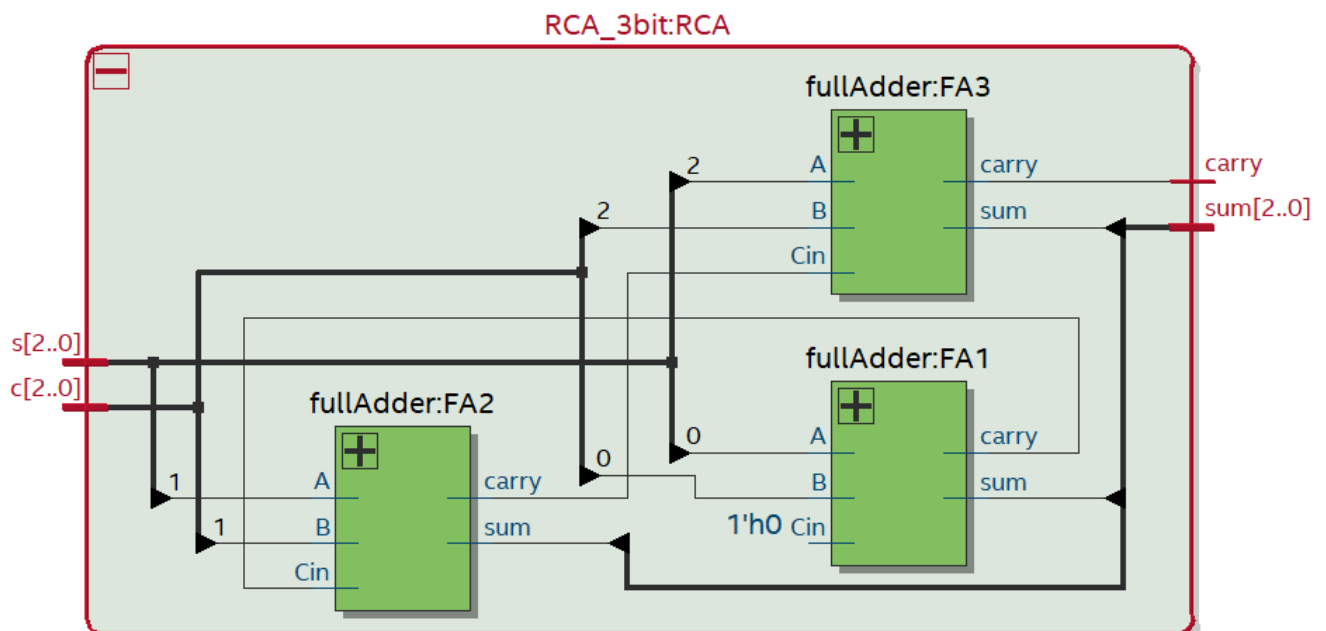
1.implement RCA\_3bit Entity by using 3FullAdder



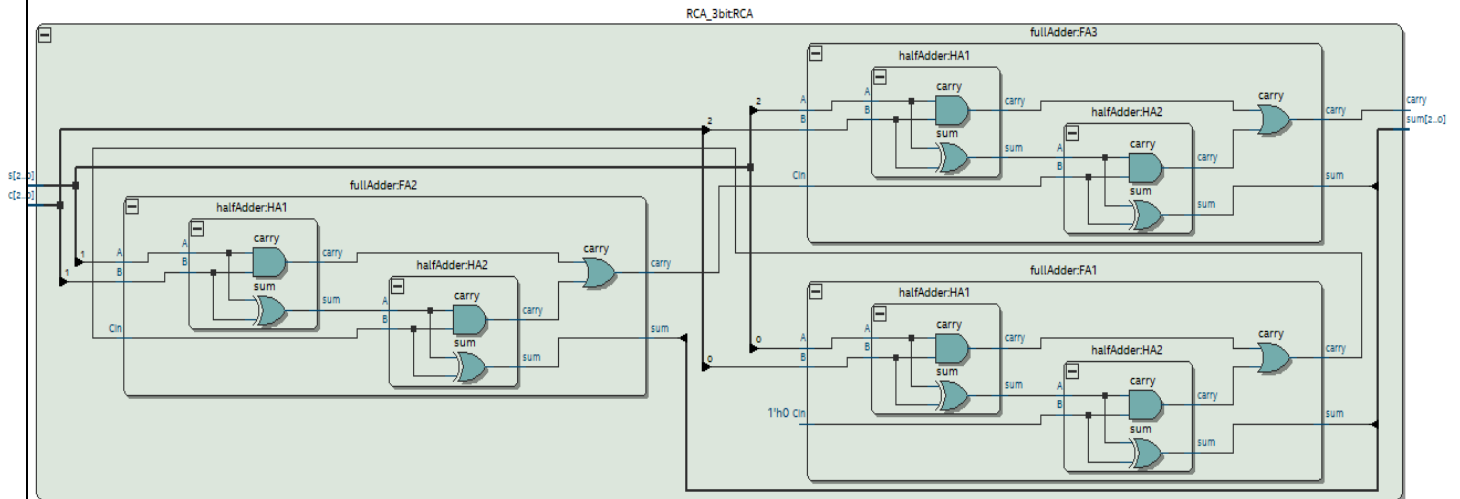



2.implement HalfAdder:

## halfAdder:HA1

 

3.implement stage2 by using RCA and HA:



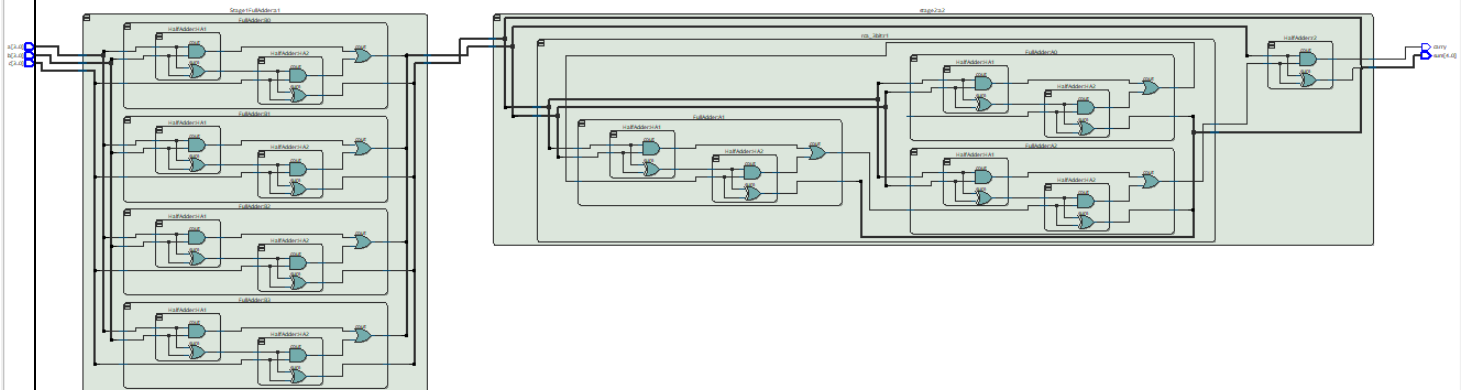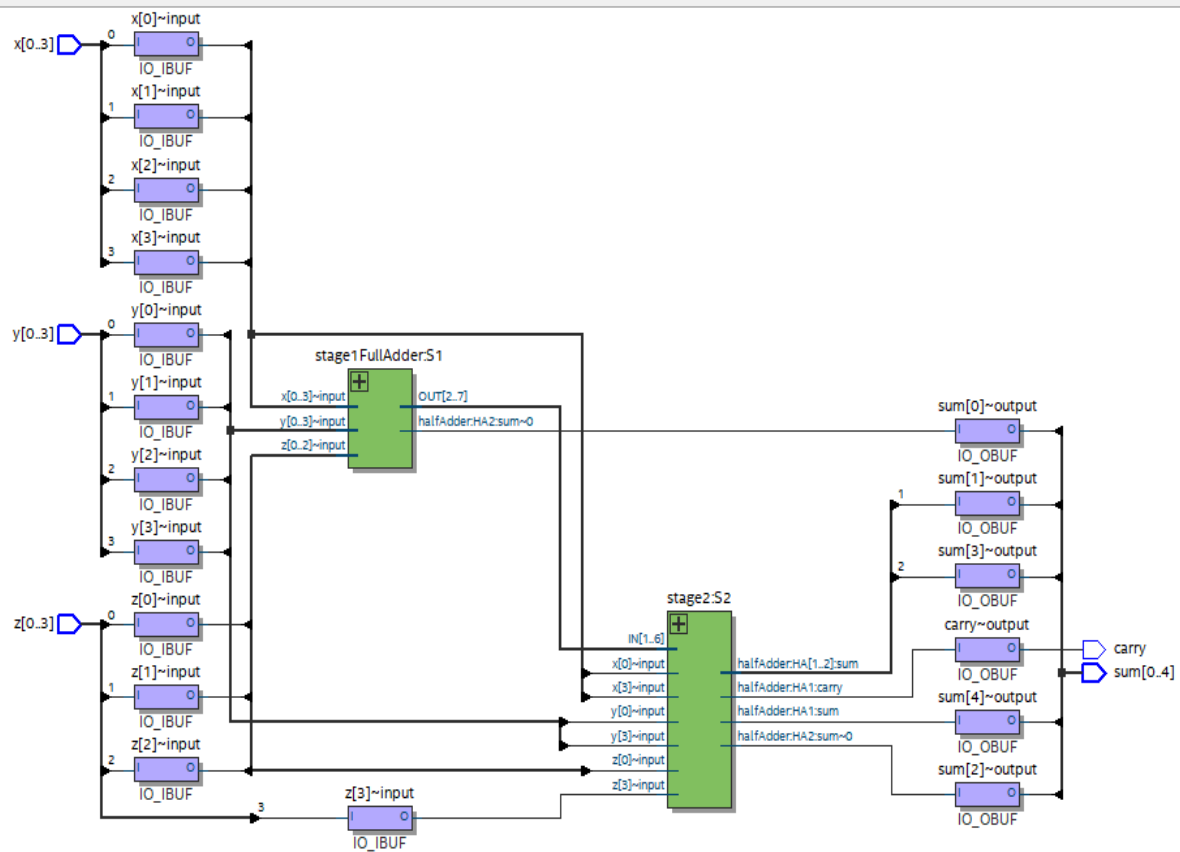

In our Quartus file we have 6Entites:


- 1.HA
- 2.FA
- 3.RCA
- 4.stage1(4fullAdder)
- 5.stage2(RCA and HA)



## 6.the Project(concatenate stage1 and stage2)final Results

And have Test bench file, and testing 3 tuples

\*Wave:

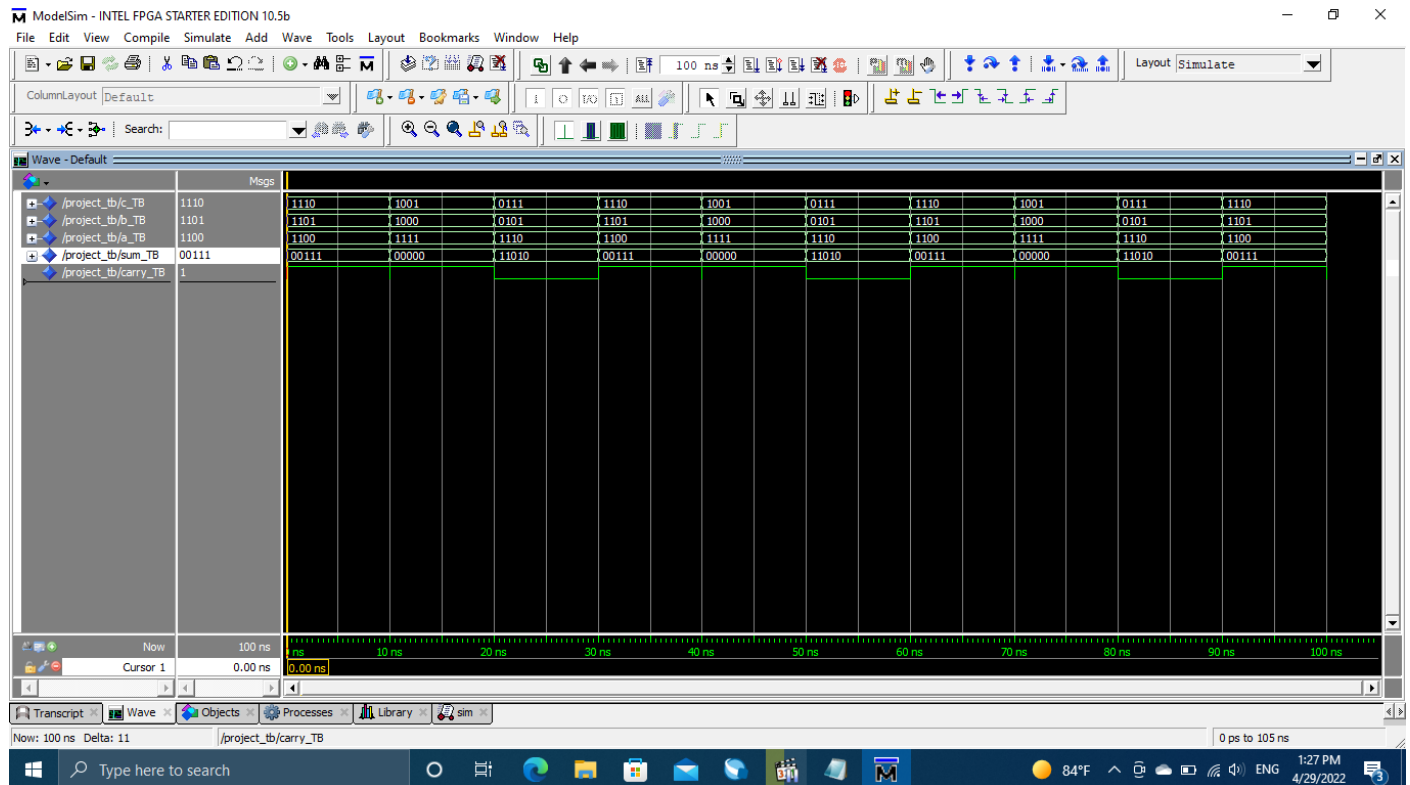

**DONE PROJECT**

**Group Names:**

**1.Hafsa Khanfar 201810054**

**2.Raja' Asad 201911051**

**3.Nada Obaid 201911089**